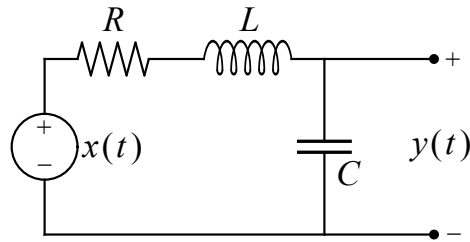




Consider a circuit consisting of a (variable) voltage source, a resistor, an inductor and a capacitor wired in series, as shown below.



This is an example of an *RLC circuit*, and in this project we will investigate the role such a circuit can play in signal processing. We will consider the (time dependent) voltage source $x(t)$ as the input signal to the circuit, and the voltage $y(t)$ across the capacitor as the output.

If we let $I(t)$ denote the (clockwise) current through the circuit, then the voltages across the resistor, inductor and capacitor are $RI(t)$, $LI'(t)$ and $y(t)$, respectively. According to Kirchoff's law, these voltages must add up to the input voltage, so that

$$RI(t) + LI'(t) + y(t) = x(t). \quad (1)$$

If $q(t)$ denotes the charge on the capacitor, then $q(t) = Cy(t)$. Since $I(t) = q'(t)$, this means that $I(t) = Cy'(t)$ and $I'(t) = Cy''(t)$. Substituting these into (1), we find that the input signal $x(t)$ and output signal $y(t)$ are related by the second order linear differential equation

$$LCy''(t) + RCy'(t) + y(t) = x(t). \quad (2)$$

We will assume that the input signal is $2p$ -periodic, piecewise smooth, and equal to its Fourier series:

$$x(t) = a_0 + \sum_{n=1}^{\infty} \left(a_n \cos \left(\frac{n\pi t}{p} \right) + b_n \sin \left(\frac{n\pi t}{p} \right) \right). \quad (3)$$

One can easily show that the solutions to the complementary equation

$$LCy''(t) + RCy'(t) + y(t) = 0$$

all decay exponentially as $t \rightarrow \infty$, i.e. only contribute transient terms to the output signal $y(t)$. If we furthermore assume that enough time has passed so that these transient contributions have died out, we find that $y(t)$ is also $2p$ -periodic, and so has a Fourier series:

$$y(t) = c_0 + \sum_{n=1}^{\infty} \left(c_n \cos \left(\frac{n\pi t}{p} \right) + d_n \sin \left(\frac{n\pi t}{p} \right) \right). \quad (4)$$

Exercises

Exercise 1. By directly substituting the series expressions (3) and (4) into (2), and then comparing the Fourier coefficients of both sides, express c_0 , c_n and d_n in terms of a_0 , a_n and b_n . You may assume $y(t)$ is sufficiently smooth for its Fourier series to be twice-differentiated term-wise.

Exercise 2. Create a Maple document which plots (partial sums of) the input and output signals. In order to make your code as portable as possible, it is required that:

- The values for R , L , C and p are stored in variables with these names.
- The coefficients a_n , b_n , c_n and d_n are functions of n , i.e. can be called as $\mathbf{a(n)}$, $\mathbf{b(n)}$, $\mathbf{c(n)}$ and $\mathbf{d(n)}$.
- The variable \mathbf{N} is used to specify the length of the partial sums that are plotted.
- Your plots extend from $t = 0$ to $t = 6p$.
- Your code is carefully documented and written so that the various input parameters are easily modified.

Exercise 3. With the values $R = 0.08$, $L = 0.01$, $C = 5.0 \times 10^{-5}$ and $p = 1/30$, use your code to produce plots for the following input signals.

- a. A square wave of amplitude 1
- b. A sawtooth wave of amplitude 2
- c. A triangle wave of amplitude 5

Exercise 4. The amplitude of a wave of the form $a \cos(\omega t) + b \sin(\omega t)$ is given by $A = \sqrt{a^2 + b^2}$. Use the results of Exercise 1 to show that the amplitude A'_n of the n th summand of the output series (4) is related to the amplitude A_n of the n th summand of the input series (3) by the equation

$$A'_n = \frac{A_n}{\sqrt{(1 - LC\omega_n^2)^2 + R^2C^2\omega_n^2}}, \quad (5)$$

where $\omega_n = n\pi/p$.

Exercise 5. For the values of R , L and C given in Exercise 3, plot the function

$$f(\omega) = \frac{1}{\sqrt{(1 - LC\omega^2)^2 + R^2C^2\omega^2}}$$

over an appropriate domain. In light of the relationship (5), explain why this type of RLC circuit is referred to as a *filter*. Where does the maximum of $f(\omega)$ occur in general? How is this connected to the “filtering” property of the RLC circuit?

Instructions

- You may work in a group of up to 4 students. Each student in a group is expected to contribute equally to the project. If you feel that one of your group members is not doing his share, please let me know.
- Your written solutions to the exercises must be typed and submitted as a PDF file. Diagrams produced using Maple must be included in the body of this document. The file you submit should be named using the convention `Project1_lastname(s).pdf`.
- Your Maple code must be submitted as a separate worksheet file, named using the convention `Project1_lastname(s).mw`.
- Your PDF and Maple documents must be uploaded to <http://tlearn.trinity.edu> by 5pm on March 3. Please only upload one copy of each document per group. Late projects *will not be accepted*.
- Failure to adhere to these guidelines will be penalized. If you have any questions or concerns, please ask me.